

LM3525,LM3622

A USB-Powered Lithium-Ion Battery Charger



Literature Number: SNVA520

Application Brief

A USB-Powered Lithium-Ion Battery Charger

Application Brief 101

Brian Conner


The Universal Serial Bus has become one of the most widespread and convenient ways to connect electronic devices to the PC. Countless modern portable products with built-in USB connectors readily use the USB data bus to transmit and receive data to and from PCs, but many of these battery-powered units still use a separate power supply for battery charging (often a charging cradle or a simple AC/DC converter). Sometimes overshadowed by its data bus partner, each USB connection also contains a power bus. With a maximum power rating 5.25V/500 mA, the USB power bus is a great source for charging a single-cell Lithium-Ion battery. The circuit in Figure 1 shows how to build a USB-powered single-cell Li-Ion battery charger using National Semiconductor's LM3622 Li-Ion Battery Charger Controller.

Circuit uses existing USB power-bus to charge a single-cell Li-Ion battery.

The battery-charger circuit is designed to operate as a high power USB function. To be compliant with USB Specifications (Rev. 1.1), a high-power function must not draw more than 500 mA from the bus during normal operation. The LM3622 uses the 0.25Ω current-limit resistor R_1 to set a 400 mA maximum charging current. This leaves a 100 mA surplus that can be used to supply USB control circuitry and other functions in the device.

There are additional current restraints on a high-power USB function that apply during system start-up or when a device is initially connected to an active bus. Until a device is properly configured by the USB system, the device may not draw more than 100 mA

Figure 1: A USB-powered Lithium-Ion Battery Charger.

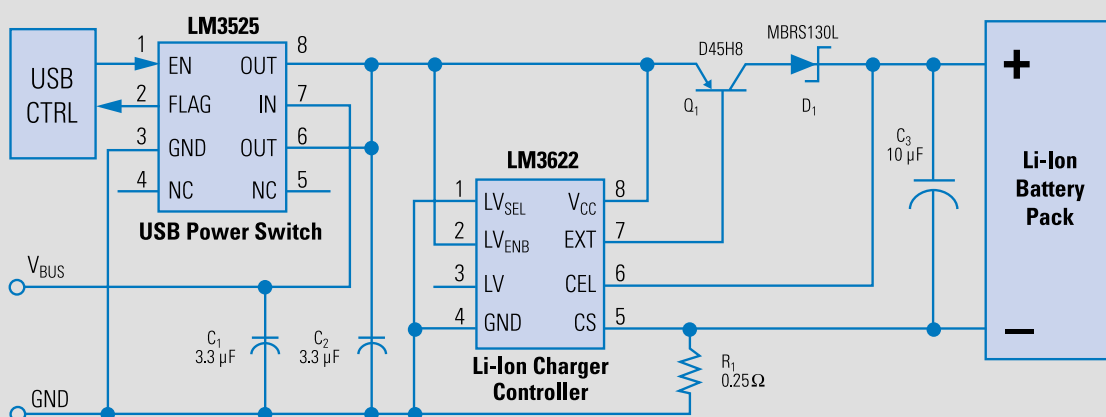

Advertisement

from the bus. In the above design, National Semiconductor's LM3525 USB power switch keeps the battery charger circuit isolated from the bus during start-up so that the charge current does not overload the bus. When the port is properly enumerated, a USB control signal enables the LM3525 switch, connecting USB power (V_{BUS}) to the charger circuit. In addition to on-and-off switching, the LM3525 provides over-current and under-voltage protection to the design.

A circuit designed with minimum voltage drop will allow the charger to function at the low USB power-bus voltage.

The voltage drop between the bus supply, V_{BUS} , and the charger circuit should be carefully considered in designing a USB battery charger. The circuit's transistor, Q_1 (D45H8), and diode, D_1 (MBRS130L), were chosen for their low-dropout properties so that the circuit could charge the battery even under low input voltage conditions. With these preferred components, the voltage drop between the LM3525 input and the battery cathode must be 530 mV (typ.) or greater for the circuit to deliver the full 400 mA charge current to the battery. For an optimal charge time, the maximum charge current should be delivered to the battery until the battery reaches its full-charge voltage. With a 4.2V Li-Ion battery, this would require the voltage at the input to this charging circuit to be above 4.7V (typ.). The USB specification sets the minimum output supply voltage at 4.75V, but then provides for resistive drops in the USB cable and connectors up to 350 mV. Thus, in the absolute worst case, the voltage at the input to the charge circuit could be as low as 4.4V and still be within USB specifications, limiting the effectiveness of the charging circuit.

Put clearly, a system with a USB supply voltage on the low end of the specification can slow a battery charge, or even prevent a full battery charge altogether. Optimal charge times of a 4.2V battery will occur when the input voltage of the charge circuit is at or above 4.7V (typ.).

When the input voltage of the circuit falls to 4.6V and the battery nears its fully charged voltage of 4.2V, there is not sufficient voltage across Q_1 and D_1 to deliver the full charge current. With only 400 mV across Q_1 and D_1 , these components are squeezed so they cannot pass more than 200 mA to the battery. The available charge current has been reduced by 50% as a result of the low input voltage, extending the time it takes to "top off" the battery with constant-voltage charging.

The battery will not even reach the full 4.2V charge when the input voltage falls below 4.5V. With a well designed USB supply using low-impedance connections and cables, however, the voltage at the input to the charging circuit should be high enough that the slow or incomplete charges mentioned here will not occur.

Thus, the circuit presented is able, under most conditions, to utilize the power-supplying capabilities of the USB bus to provide easy and convenient Lithium-Ion battery charging.

Visit The National Edge, our on-line technical journal, for an expanded version of this Application Brief
edge.national.com

Data Sheet Download

<http://www.national.com/pf/LM/LM3622.html>
<http://www.national.com/pf/LM/LM3525.html>

National Semiconductor
2900 Semiconductor Dr.
PO Box 58090
Santa Clara,
CA 95052-8090
1 800 272 9959

Visit our Web site at:
www.national.com

For more information,
send Email to:
support@nsc.com

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Mobile Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Transportation and Automotive	www.ti.com/automotive
Video and Imaging	www.ti.com/video

TI E2E Community Home Page

e2e.ti.com

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2011, Texas Instruments Incorporated